Kathmandu University Department of Electrical and Electronics Engineering ANALOG ELECTRONICS LABORATORY WORK

EXPERIMENT 5: Frequency Response of an Amplifier

Objectives: To understand the frequency limitation of an amplifier.

Software:

Multisim 8

Theory:

Based on signal frequency an amplifier can be classified into four types. *DC amplifier* amplifies very low frequency. *Audio amplifiers* have good frequency response over the audio frequency range. *Video amplifiers* (wide band amplifiers) have frequency range from DC to few MHz *RF amplifiers* (Front end amplifiers) have tuned or wideband type of frequency response.

Amplifiers are limited in the higher portion of spectrum because of stray and parasitic capacitance effect (which is unavoidable⁽²⁾). For example when the operating frequency increases, C_i shunts most of the signal current to ground though C_i and C_o have very low value of capacitance. Gain of amplifier reduces in the higher portion of spectrum.



Fig 1

Amplifiers are limited in the lower portion of spectrum because of the blocking capacitances though the value of blocking capacitances is in the range of uF.



Fig 2

The gain of a STC (Single Time Constant) network rolls-off by 20dB/decade or 6dB/octave in the stop band. There will be a phase lag between the output voltage and input voltage waveform.

In Multisim® software package, one can use Bode plotter to view the frequency response of any amplifier. In this lab we will see the frequency response of a VCVS.

STC Network



Procedure

- 1. Connect the circuit as shown in fig 3.
- 2. Feel free to use various controls of the Bode plotter. (Especially Crosshair)
- 3. Determine the break frequency. (-3dB point)
- 4. Notice the phase shift. (Positive or negative?)
- 5. Change the resistor by capacitor and capacitor by resistor.
- 6. Determine the break frequency.
- 7. Notice the phase shift. (Positive or negative? ©)

High Frequency Response of an Amplifier



Procedure

- 1. Connect the circuit as shown in fig 4.
- 2. Feel free to use various controls of the Bode plotter.
- 3. Sketch the magnitude response of the amplifier.
- 4. Find the DC gain of the amplifier.
- 5. Find the bandwidth of the amplifier (3dB point). Compare it with the theoretical result.

- 6. Sketch the phase response.
- 7. Remove the capacitors and again find the DC gain of the amplifier (K_o).
- 8. Note the phase plot.
- 9. Decrease the input capacitance to 5pF and find the bandwidth of the amplifier. Compare it with 5.
- 10. Increase the input capacitance to 100pF and find the bandwidth of the amplifier. Compare it with 5.
- 11. Decrease R_i to 5K and find the bandwidth and DC gain of amplifier.
- 12. Remove the output 10pF capacitance and find the BW of the amplifier. Compare it with the theoretical result.
- 13. Connect the 10pF capacitor in its own place. Increase its value to 100pF and find the BW of the amplifier.

Low Frequency Response of an Amplifier



Procedure

- 1. Connect the circuit as shown in fig 5.
- 2. Sketch the magnitude response and the phase response.
- 3. Determine the break frequency. $f = \frac{1}{2\pi(R_s + R_i)C}$. Please note that

 $R_s + R_i$ is the effective resistance across the capacitor.