

## EXPERIMENT 8: MOS Field Effect Transistor Characteristics

**Objectives:** To understand E-MOS characteristics and design a simple inverter and amplifier using an N-MOS

**Software**  
Multisim 8

**Theory:**

In the NE-MOS of fig 1, when  $v_{GS}$  is less than  $v_t$ , the drain current  $i_D$  is zero irrespective of the applied drain potential because of two diodes connected in back to back fashion. When  $v_{GS}$  is higher than  $v_t$ , the channel gets induced and maintains uniform depth for small  $v_{DS}$  (less than 50 mV). The uniform channel is shown by dotted line in fig 1. MOS acts as a linear resistor whose resistivity is controlled by the overdrive voltage. When  $v_{DS}$  is increased, uniformity of channel depth is lost at the drain end and the channel gets completely blocked when  $V_{DS} = V_{GS} - V_t$ .

$$V_{DS} < V_{GS} - V_t \text{ (Triode Region, VCR region)}$$

$$V_{DS} \geq V_{GS} - V_t \text{ (Saturation Region, Linear amplification region)}$$

The volt ampere characteristic of E-MOS in triode region is given by (1) and in saturation region is given by (2).

$$i_D = K'_n \frac{W}{L} \left[ (v_{GS} - v_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right] \quad (1)$$

$$i_D = \frac{1}{2} K'_n \frac{W}{L} [(v_{GS} - v_t)^2] \quad (2)$$

The ratio  $W / L$  is called the aspect ratio of MOSFET.  $K'_n = \mu_n C_{ox}$ .

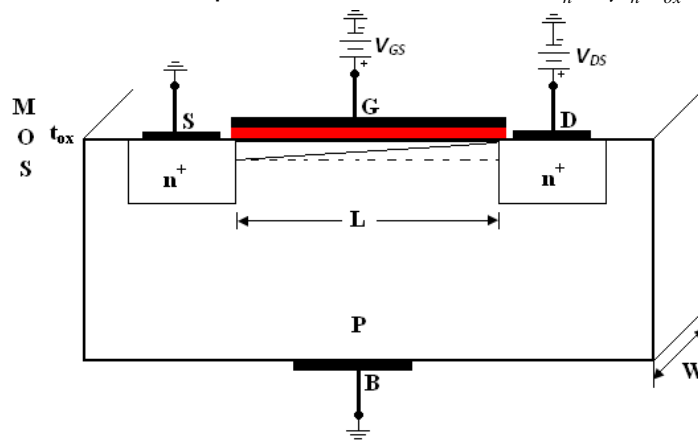


Fig: 1

## VTC of NMOS Inverter

The VTC of NMOS inverter in fig 4 is shown in fig 2. In the region XA, MOS is in the cut-off region. MOS enters saturation in AQB and the output voltage falls by square law relationship given by (3).

$$v_O = V_{DD} - \frac{1}{2} K_n' \frac{W}{L} (v_I - v_t)^2 R_D \quad (3)$$

Gain of MOSFET in AQB is given by  $-g_m R_D$ , where  $g_m = K_n' (W/L) V_{OV}$ . We have neglected the channel length modulation effect. For small signal operation  $v_{gs}$  around the quiescent should be  $\ll 2V_{OV}$ .

In BC, MOS operates as almost linear resistor. The output voltage falls as given by (4).

$$v_O = V_{DD} \frac{r_{DS}}{r_{DS} + R_D} \quad (4)$$

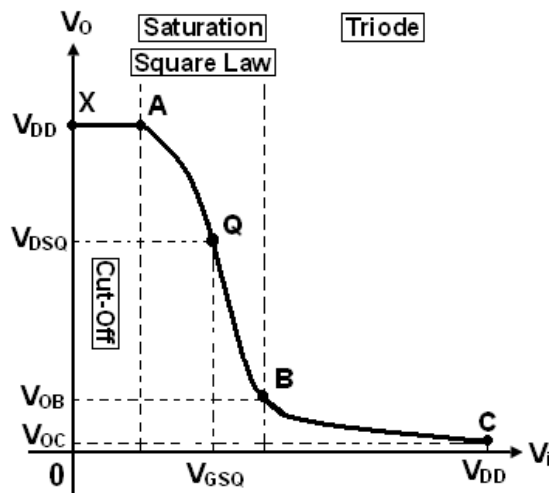


Fig: 2

## Volt Ampere Characteristics

### Procedure

1. Connect the circuit as shown in fig 3 (a). Set 3TEN Virtual MOSFET parameters as,  $W=10\mu\text{m}$  and  $L=1\mu\text{m}$ ,  $V_{TO}=0.7$ ,  $K_P=100\text{e-}6$ .
2. Complete table 1.

$V_D$	Operating Region	$I_D$ $L=1$	$I_D$ $L=0.5$
0.5			
0.9			
3			

Table: 1

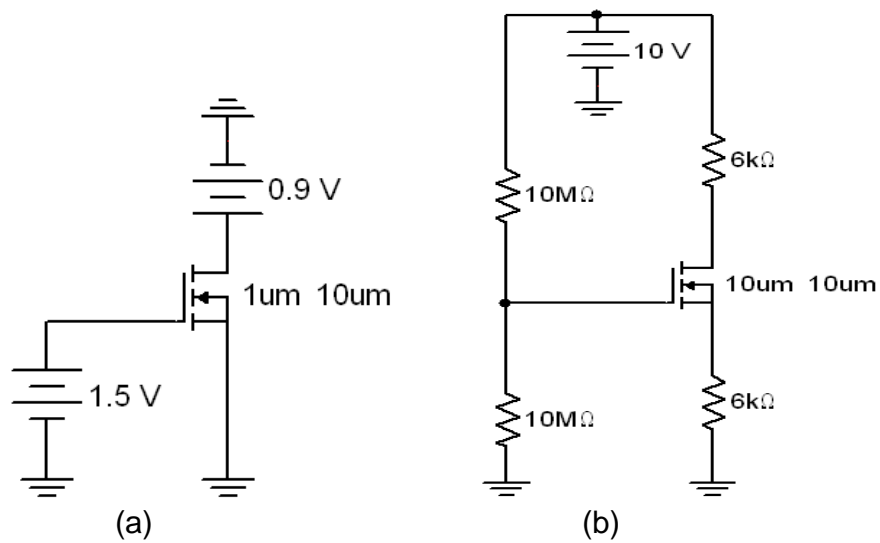


Fig: 3

3. Connect the circuit as shown in fig 3 (b).  $W=10\mu m$  and  $L=10\mu m$ ,  $V_{TO}=1$ ,  $KP=1e-3$ .
4. Complete table 2. While calculating theoretical values assume that the MOSFET is working in the saturation region.

Result	$V_G$	$I_D$	$V_S$	$V_{GS}$	$V_D$	$V_{DS}$	$I_G$	$I_S$
Theoretical								
Software								

Table: 2

### MOS Resistive Switching Characteristics

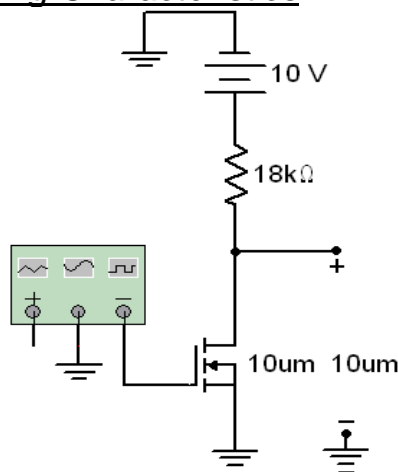


Fig: 4

### Procedure

1. Connect the circuit as shown in fig 4.  $W=10\mu m$  and  $L=10\mu m$ ,  $V_{TO}=1$ ,  $KP=1e-3$ .
2. Set the FG as 1 kHz, 5 V amplitude with 5 V offset, sine.

3. Connect CH1 of OSC to input and CH2 to output. See in YT mode the switching characteristics of MOSFET. Use DC coupling mode.
4. Change the oscilloscope display format to XY mode. The VTC will be seen like as shown in fig 5.

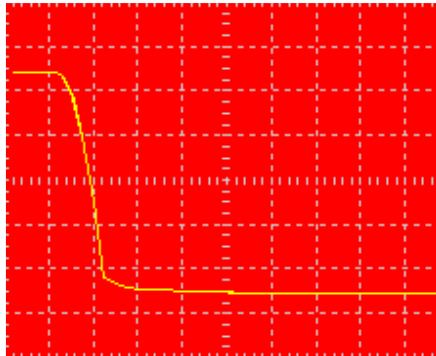


Fig: 5

5. With reference to fig 5 and fig 2 complete table 3.

Result	X	A	$V_{IB}$	$V_{OB}$	$V_{OC}$	Q
Theoretical						
Software						

Q should be selected to give maximum signal swing @ the output

Table: 3

### MOS Amplifier Characteristics

#### Procedure

1. Remove FG and Oscilloscope from fig 4.
2. Give 1.816 V as the gate potential.
3. Complete table 4.

Result	$V_{DSQ}$	$I_{DQ}$
Theoretical		
Software		

Table: 4

Region of Operation: \_\_\_\_\_

Overdrive Voltage: \_\_\_\_\_

4. Set the FG as 1 kHz, 1 mV amplitude with 1.816 V offset, sine.
5. Use AC coupling mode of oscilloscope. CH1=Input, CH2=Output.
6. Find the gain of amplifier.
7. Sketch amplifier characteristics in XY mode.

